

Big Book of RF Engineering Notes

Table of Contents

1. [Noise](#)
2. [Signal Distortion](#)
3. [Amplifiers](#)
4. [Oscillators](#)
5. [Mixers](#)
6. [Impedance Matching](#)
7. [Microwave Structures](#)
8. [Modulation and Coding](#)
9. [Mixed Signal Systems](#)

Noise in RF Systems

Thermal noise floor is kT_0B , which is the noise power produced by a matched resistor at the IEEE reference temperature $T_0 = 290K$ over a bandwidth of B . If the bandwidth is 1Hz, then the thermal noise floor is -174dBm/Hz .

IEEE definition of noise figures (NF) or noise factor (F) are as follows:

$$F = \frac{\text{SNR}_{in}}{\text{SNR}_{out}} \quad (1)$$

$$\text{NF} = 10 \log_{10}(F) \quad (2)$$

where SNR_{in} is the signal-to-noise ratio at the device input, when the input noise is thermal-limited. In other words, the input noise power is equal to the noise power produced by a matched resistor at a physical temperature of $T_0 = 290K$.

Example: Measurement of Amplifier Noise Figure Using Cold Source

In this section, we discuss the noise figure measurement of an RF low-noise amplifier using the cold source method. We will use the TinySA spectrum analyzer and the NanaVNA vector network analyzer. The device under test is the Nooelec LaNA HF, which is an LNA covering the 50kHz to 150MHz band.

With the cold source method, we first measure the gain of the amplifier using the VNA.

...

Next, we measure the noise power generated by the amplifier. We first put a 50Ω termination directly at the input port of the TinySA. We measure a noise floor of -169.3dBm/Hz . Since the thermal noise floor is $10 \log_{10}(1.38 \times 10^{-23} \times 10^3 \times 290) = -173.9\text{dBm/Hz}$, we conclude that the noise generated by the internal circuitry of the TinySA increased the total noise power by approximately 4.6dBm/Hz . This means the noise figure of TinySA is about 4.6dB. Alternatively, we can say it has an effective noise temperature of approximately $290 \left(10^{4.6/10} - 1\right) = 546.4K$, referred to the inputs.

Having characterized the noise properties of the TinySA, we can now measure the DUT cascaded with its internal receiver. We will then remove the added noise of the TinySA from the overall measurements, to obtain the noise figure of the DUT itself.

Noise Cascade

When multiple noisy stages are cascaded, the total effective noise temperature referred to the input of the first stage is given by:

$$T_{sys} = T_1 + \frac{T_2}{G_1} + \frac{T_3}{G_1 G_2} + \dots \quad (3)$$

Where T_n is the effective noise temperature of the n^{th} stage, *referred to its own input*. Moving the reference location of an effective noise temperature value can be done by simply multiplying/dividing the gains of the appropriate stages. In [3], it can be seen that the noise temperature of the very first stage dominates the total temperature, if there is large gain afterwards. Hence in a receiver it is desirable to put an LNA as close to the antenna as possible, to reduce the impact of noise in the later stages.

We can also calculate the noise figure of the entire system. Each stage of the system will have its own specified noise figure. Remember that the noise figure [2] is defined for when the input noise power is equal to exactly kT_0B . So we cannot simply cascade the noise figures of the individual components together, because the input to the latter stages are no longer a matched resistor. Instead, it is safer to calculate the effective noise temperature of each stage using its specified noise figure, cascade the temperatures together using [3], then convert the total temperature back to a total noise figure:

$$F_{sys} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots \quad (4)$$

Signal Distortion

Sources of nonlinear signal distortion:

- Gain compression
- Intermodulation

Amplifier

Specifications

Efficiency

Linearity

Junction Temperature

Linearity

Biasing

Flatness

Isolation


Stability

Unstable amplifiers will oscillate: they will output spurious signals even when there is no input. This is because noise in the amplifier circuit can be amplified through positive feedback at the oscillation frequencies. The spurs can be problematic even if they do not fall inside the frequency band of operation because:

- They can mix with other signals, generating in-band noise/distortion
- If they are very high in amplitude, they can saturate the amplifier, reducing the gain of the desired in-band signal

An amplifier circuit is **unconditionally stable** if:

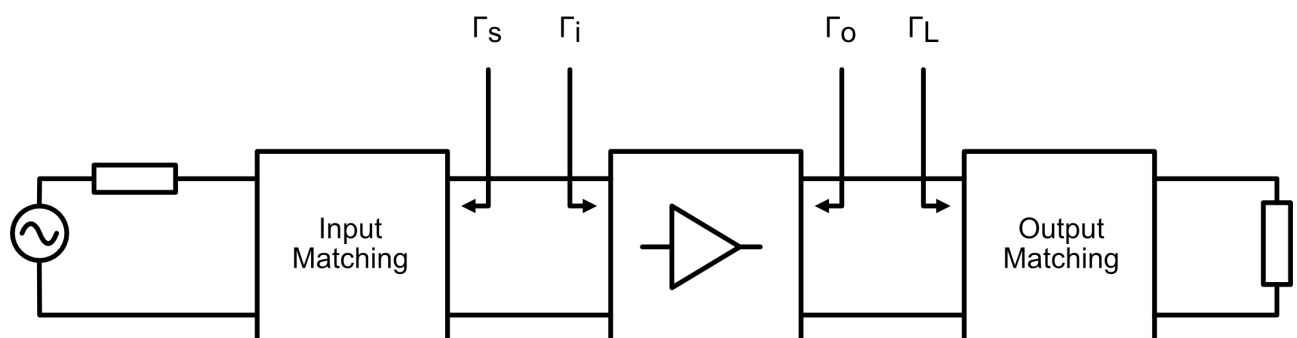- The reflection coefficient seen into the input (Γ_i) is smaller than 1 for ANY passive load.
- The reflection coefficient seen into the output (Γ_o) is smaller than 1 for ANY passive source impedance.



We can tell if an amplifier circuit will be stable or not by looking at the input and output stability circles.

Noise Figure

Hybrid Amplifier

Oscillators and Phase Noise

We can model the output voltage of a noisy oscillator as:


$$v(t) = A(t) \cos[\omega_c t + \phi_n(t)] \quad (5)$$

where $A(t)$ captures amplitude noise, and $\phi_n(t)$ captures the phase noise.

We can interpret phase noise as phase modulation of the desired ideal oscillator output signal $\cos(\omega_c t)$, except that the modulation signal is pure noise. For simplicity, let us first consider the case when the phase modulation is a single-tone sinusoid. This is a helpful example, since we can interpret a noisy signal as the summation of infinitely many sinusoids all with random amplitudes and phases.

Effect of Phase Noise on EVM in OFDM Systems

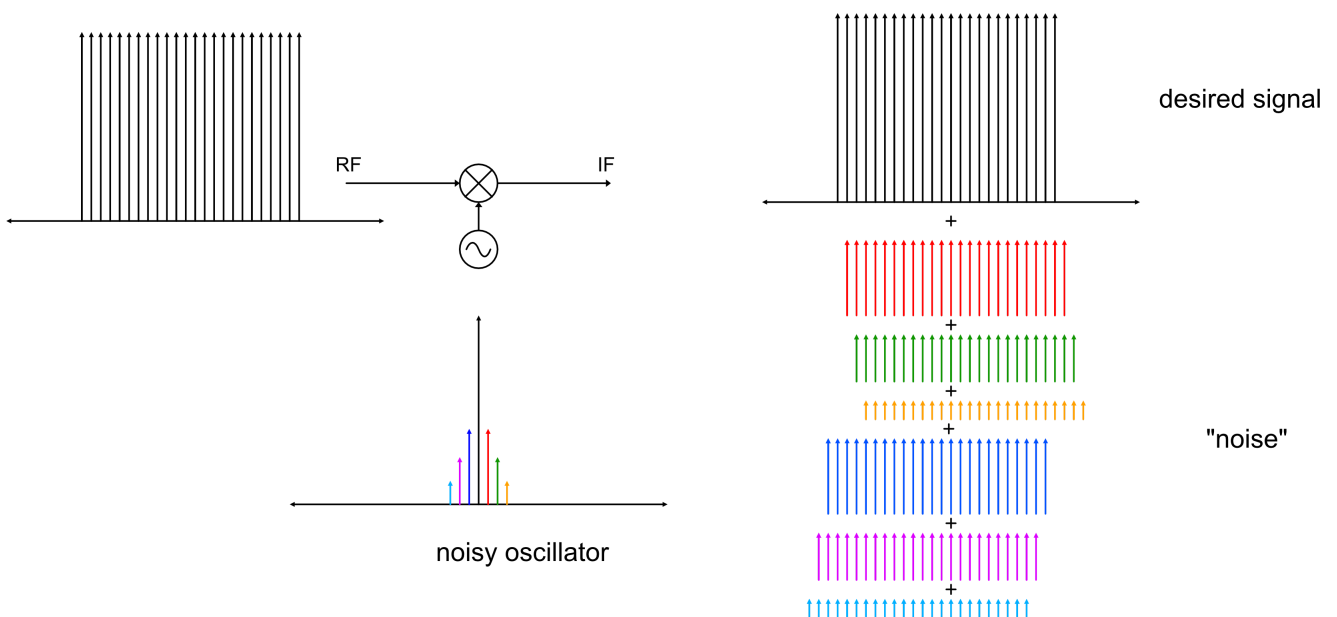The effect of phase noise on the EVM of an OFDM signal can be interpreted as follows.



Instead of getting a clean copy of the down-converted (or up-converted signal), we get a bunch of shifted copies of the signal added on top of the desired signal, caused by the side bands of the noisy oscillator. Since each subcarrier is uncorrelated with the others, these additional copies of the signal act as noise.

The total effective "noise" power added on top of each subcarrier can be determined by the total integrated phase noise. For example, if the single-sideband integrated phase noise is -40dBc, then the total EVM contribution of the noisy oscillator is -37dBc (+3dB since there are two sidebands).

Impact on adjacent channel leakage: as can be seen by the picture above, phase noise causes power to be spilled over to adjacent channels. Unlike spectral regrowth caused by nonlinearity, the adjacent channel leakage ratio will NOT improve as we scale down the channel power. It also cannot be corrected digitally (e.g. using digital predistortion).

White Phase Noise

Consider the case where $\phi_n(t)$ is Gaussian distributed with zero mean and standard deviation σ_{rms} . This means the probability density function of $\phi_n(t)$ is given by

$$f(\phi) = \frac{1}{\sqrt{2\pi}\sigma_{rms}} e^{-\frac{\phi^2}{2\sigma_{rms}^2}} \quad (6)$$

Oscillator Pulling

Oscillator pulling happens when a strong (undesired) signal couples to a resonator, causing its resonance frequency to change. It is also called **injection locking** or **injection pulling**.


Mixers

Single Sideband Mixers

IQ Mixers

The following diagram depicts an IQ mixer used as a single-sideband (SSB) receiver, with upper sideband (USB) selection.

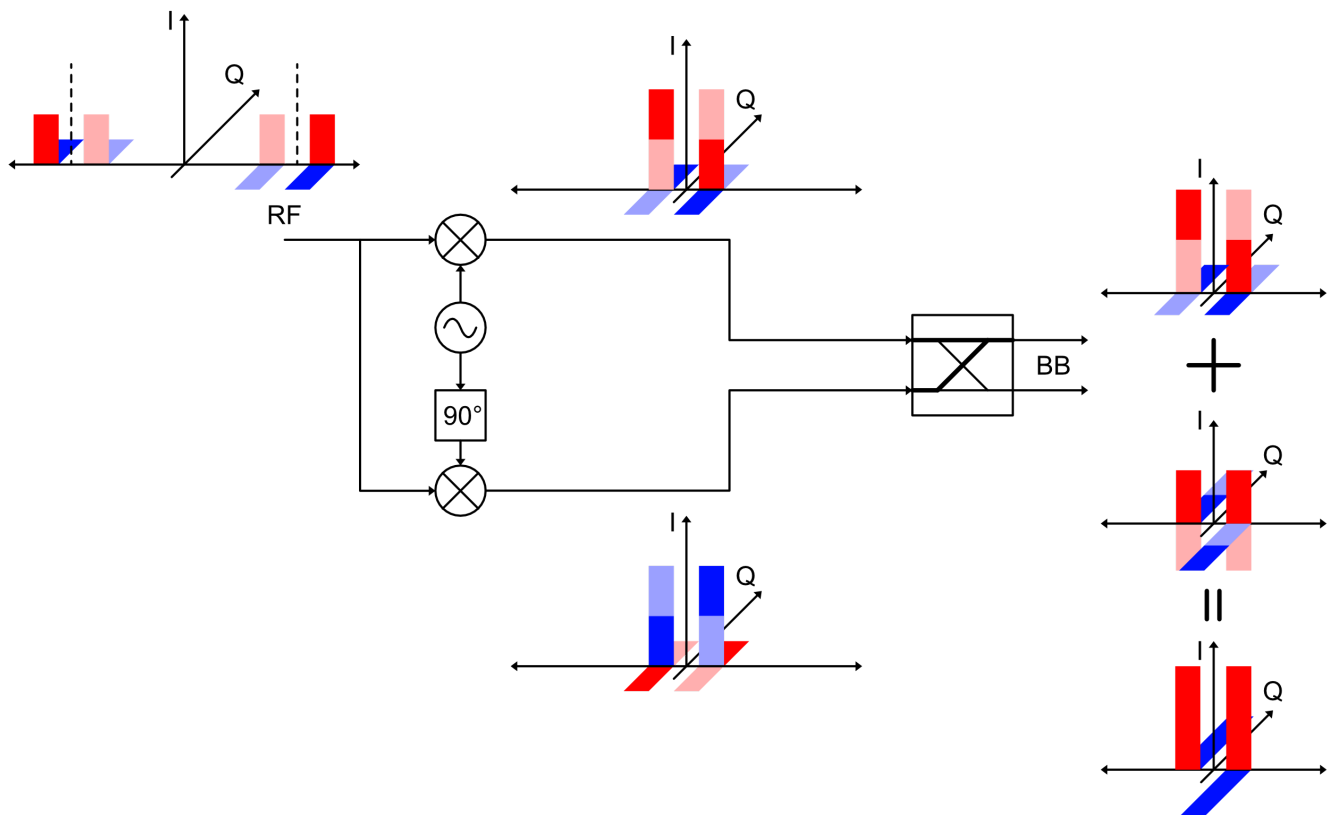Selecting the other output of the 90° hybrid would give us the lower sideband (LSB).



Recall that 90° phase shift of a signal corresponds multiplying all of the positive frequency components by $-j$ and all of the negative frequency components by j . Think about adding 90° to $\cos(\omega t)$, turning it into $\sin(\omega t)$. Now repeat for all values of ω .


In this particular example, the signal in the lower sideband destructively interferes at the output of the hybrid, leaving us with just the upper sideband.

Phase or amplitude mismatch along the signal chain will result in incomplete cancellation of the lower sideband, and attenuation of the summed upper sideband. This degrades the EVM of the output, since the lower sideband is folded on top of the upper sideband, effectively acting as noise.

Note that noise in the lower sideband behaves the same as signal, in that they add destructively at the output of the hybrid coupler. This means that the SSB IQ mixer has the same noise figure as a conventional double-sideband mixer. It does not suffer the 3dB increase in NF experienced by SSB mixers implemented using bandpass filters.

Impedance Matching

Smith Chart

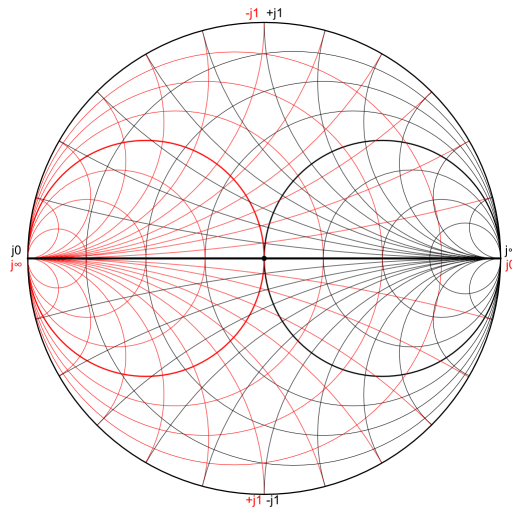



The S_{11} curves will rotate clockwise on the smith chart as frequency increases. This is related to the Foster Reactance Theorem, which states that the reactance of passive lossless one-port network must increase monotonically with frequency. In the presence of loss or mismatch, the reactance may decrease with increasing frequency, inside a limited range. Correspondingly, within that frequency range, the S_{11} curve will rotate counter clockwise on the smith chart. As a side note, we can use this technique to mimic negative capacitors or negative inductors over a finite bandwidth, achieving broadband impedance matching.

LC Components on Smith Chart

This section describes how shunt and series LC components behave on the smith chart, which can be used to intuitively derive potential matching network topologies.

Series Capacitor

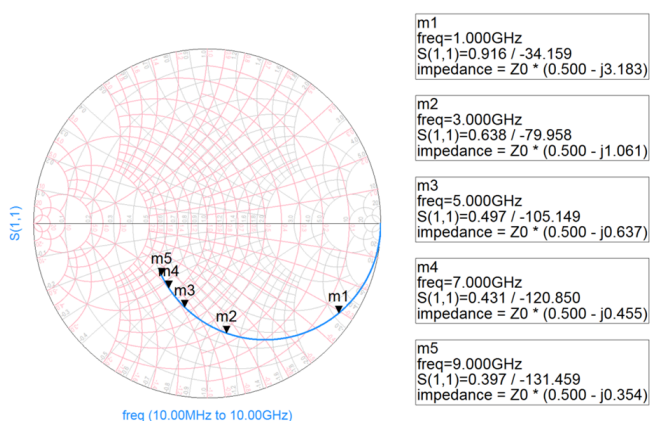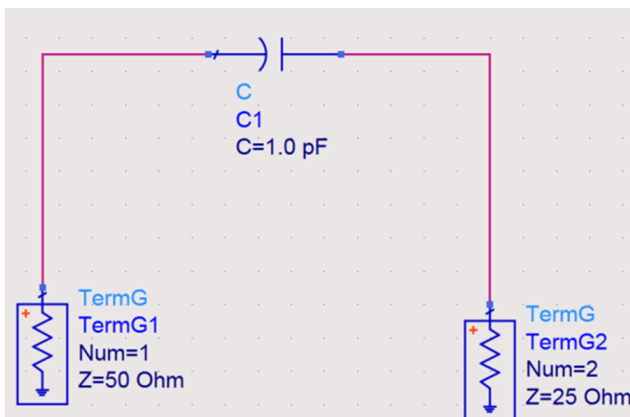
As the frequency increases from DC to infinity, the input impedance swings from open circuit (OC) to the terminating resistance.



Frequency response of series capacitor on the Smith chart.

Note that the series capacitor is a high pass circuit. This means its effect on the impedance is stronger at low frequencies, and weaker at high frequencies. This can be seen from the impedance plot on the Smith chart. The high-frequency points are far away from the right side of the Smith chart, where any tiny movement represents a huge change in impedance, as can be seen by the axis ticks.

Series Inductor

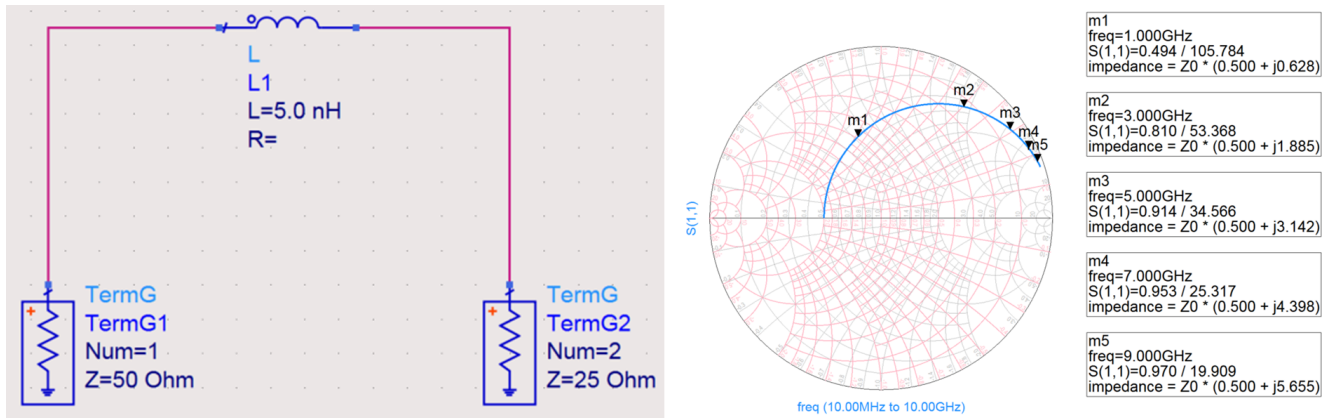


Frequency response of series inductor on the Smith chart.

At DC, the series inductor behaves as a perfectly conducting wire; hence the input impedance is just that of the terminating resistance. As the frequency increases to infinity, the input impedance swings towards OC.

The series inductor is a low pass circuit, meaning it has stronger effect to the input impedance at high frequencies. In the plot above, we see that the low frequency points are far away from the right side of the Smith chart, while the high frequency points are clustered on the right side, where any small movements represents huge deviations in the impedance.



Shunt Capacitor

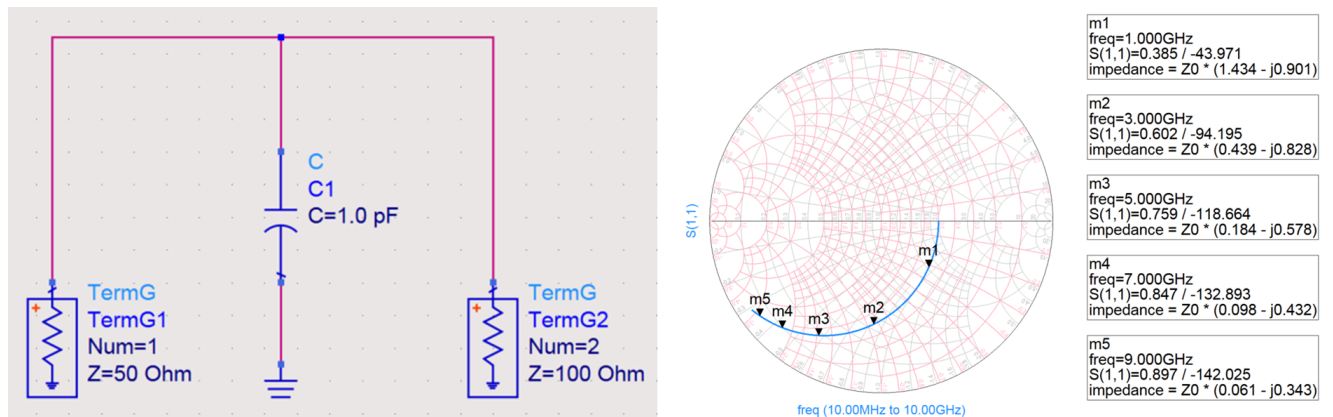

Frequency response of shunt capacitor on the Smith chart.

The shunt capacitor is a low pass circuit, meaning it will have larger impact on the admittance of the circuit at high frequencies. On the Smith chart, the high frequency points are clustered to the left side, where any small movements correspond huge changes in admittance.

Shunt Inductor

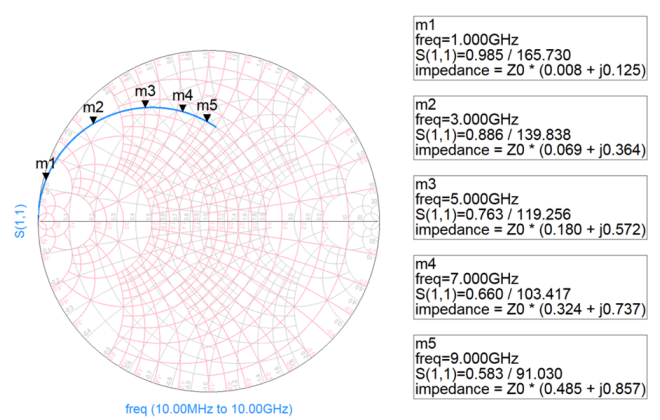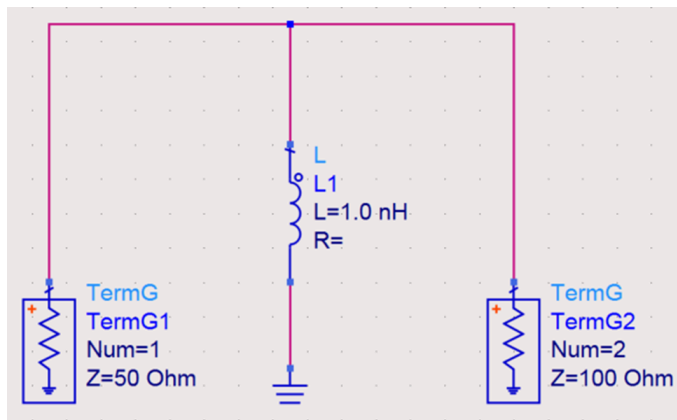

Frequency response of shunt inductor on the Smith chart.

Series RLC Resonator

Shunt RLC Resonator

Broadband Matching Techniques

Reducing Q-factor Using LC

The idea here is to twist the S_{11} trace on the Smith chart by adding components that affect the two ends, such that they become closer to the real axis. This lowers the Q factor of the network and allows us to match it over a broader bandwidth.

Via Transitions

Via transitions connect signal traces on different layers of a printed circuit board.

Modulation and Coding

Different modulation formats and code rates will require different SINAD (signal-to-noise and distortion).

Mixed Signal Systems

Digital-to-Analog Conversion

Analog -to-Digital Conversion

